

# EE230: Experiment No.8

## Logarithmic Amplifier

Aksh Garg, 20D070008

March 20, 2022

## 1 Overview of the experiment

### 1.1 Aim of the experiment

The aim of this experiment is to understand Logarithmic Amplifier using op-amps (specifically TL084) about how it works and should be the circuit to implement this type of Amplifier. In this experiment, we have to find the linear region at which we can use the given circuit for our use, given the IV characteristics of the circuit. This circuit is simulated using NgSpice software, and these simulation results needs to be compared with the theoritical results.

### 1.2 Methods


First of all, the given IV characteristics are analyzed, we find the linear region to work upon the om-amp, and by using linear regression in python, we find the slope and the y-intercept (which is required for further calculations).

After that, circuit diagrams are made using XCCircuit software of the required circuits. Now, as the circuits are formed, netlist codes are written for the circuit to completely describe the circuit and also describe what result ngspice should show to us. The readings are saved in a file and then, using this file, plots of the given parameters are made by matplotlib python script.

The lab work to be done was given in lab pdf, using that we got the circuit to be simulated.

After that, these plots were compared with the theoritical plot values and the changes are done to the circuit element values to refine the circuit.

## 2 Design

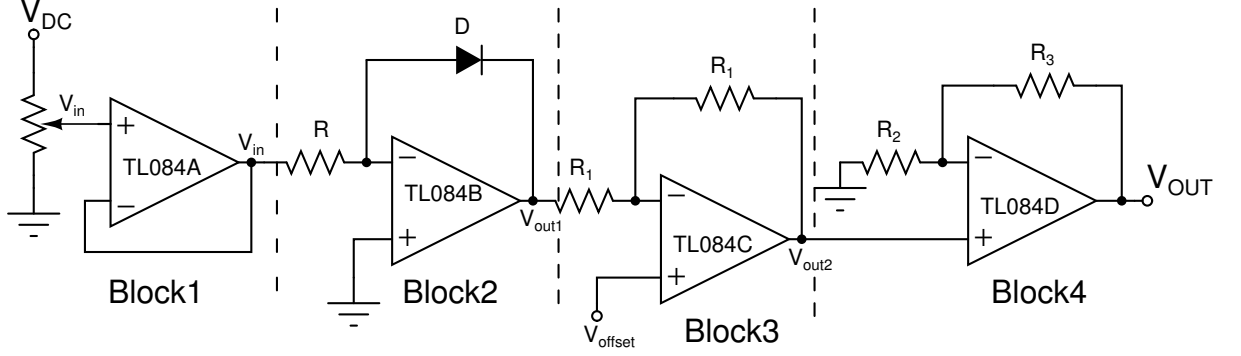

The equation for the terminal characteristics of a pn junction diode in forward bias is

$$I_D = I_S * e^{(V_D/nV_T)} \quad (1)$$

$$V_D = nV_T(\ln(I_D) - \ln(I_S)) \quad (2)$$

$$\ln(I_D) = V_D/nV_T + \ln(I_S) \quad (3)$$

$$V_{out1} = -V_D \quad (4)$$

$$V_{out1} = nV_T(\ln(I_S R) - \ln(V_{in})) \quad (5)$$

$$V_{out1} = a_1 \ln(V_{in}) + a_2 \quad (6)$$

$$a_1 = -nV_T \quad (7)$$

$$a_2 = nV_T \ln(I_S R) \quad (8)$$

We can remove the offset by subtracting  $a_2$  from  $V_{out1}$ . The result can then be multiplied by  $1/a_1$  using a suitable amplifier, to obtain at the output the true natural logarithm of  $V_{in}$ .

The third block is used for removing the offset from  $V_{out1}$ , set  $V_{offset} = a_2/2$ , so the input to block 4 would be  $-a_1 \ln(V_{in})$ .

$$V_{out} = -a_1(1 + R_3/R_2)\ln(V_{in}) \quad (9)$$

Choosing  $1 + R_3/R_2 = -1/a_1$ , we get

$$V_{out} = \ln(V_{in}) \quad (10)$$

The role of block 1 is to avoid loading the source of  $V_{in}$  by block 2.

If we assume that the maximum input voltage,  $V_{in2} = 10V$ , then  $R = 10/I_{D2}$ .

**Values:-**

By observing the readings, we got linear region  $I_D$  values from 1.266E-4 to 5.55E-4 Amperes.

So,

$$R = 10/I_{D2} = 18k\Omega \quad (11)$$

By using linear regression in this region, we got slope = 20.5409, and y-intercept = -19.30584.

$$Slope = 1/(nV_T) \quad (12)$$

$$Y - intercept = \ln(I_S) \quad (13)$$

$$n = 1/(slope * V_T) = 1.87 \quad (14)$$

$$I_S = e^{(y-intercept)} = 4.13nA \quad (15)$$

$$a_1 = -(1.87)(26)/1000 = -0.04862 \quad (16)$$

$$a_2 = (1.87)(26)\ln(4.13 * 18/1000000)/1000 = -0.46 \quad (17)$$

$$V_{offset} = a_2/2 = (nV_T\ln(I_S R))/2 = -0.23V \quad (18)$$

We set  $R_1 = 10k\Omega$ .

$$R_3/R_2 = (-1/a_1) - 1 = 19.5 \quad (19)$$

We set  $R_2 = 1k\Omega$ , and  $R_3 = 19.5k\Omega$ .

Now, we are done with all the calculations for finding the values of all the required values and parameters.

## 3 Simulation results

### 3.1 Code snippet

#### Logarithmic Amplifier

$$V_{OUT} \text{ vs } V_{IN}$$

```

.include TL084.txt
.include 1N4148.txt
x1 1 2 3 4 2 TL084
x2 0 5 3 4 6 TL084
x3 11 7 3 4 8 TL084
x4 8 9 3 4 10 TL084
r1 6 7 10k
rx 7 8 10k
r2 9 0 1.1k
r3 9 10 19.5k
r 2 5 18k
D 5 6 1N4148
vcc 3 0 15
vdd 4 0 -15
vin 1 0 dc 0
vo 11 0 -0.219
.dc vin 0 10 0.1
.control
run
plot v(10)
print v(10)
.endc
.end

```

$V_{OUT}$  vs  $\ln(V_{IN})$

This is done by using python.

### 3.2 Simulation results

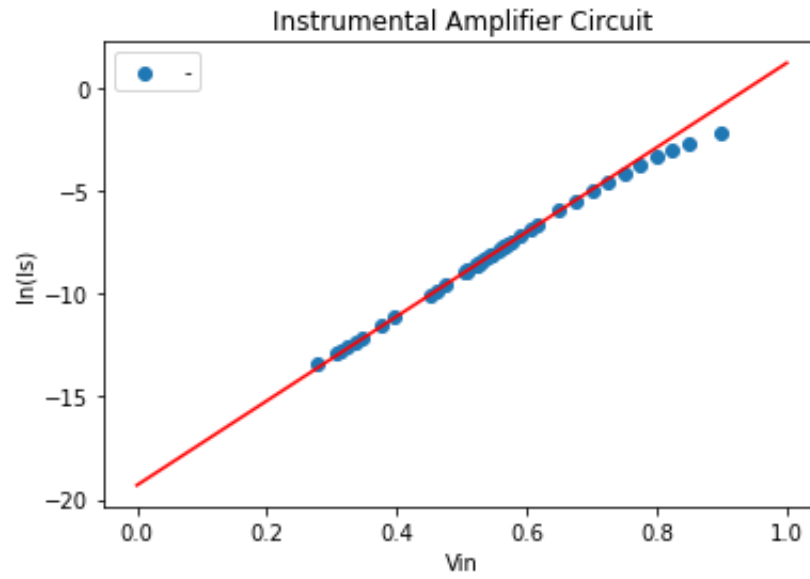


Figure 1: IV characteristics from the given data and also linear regression

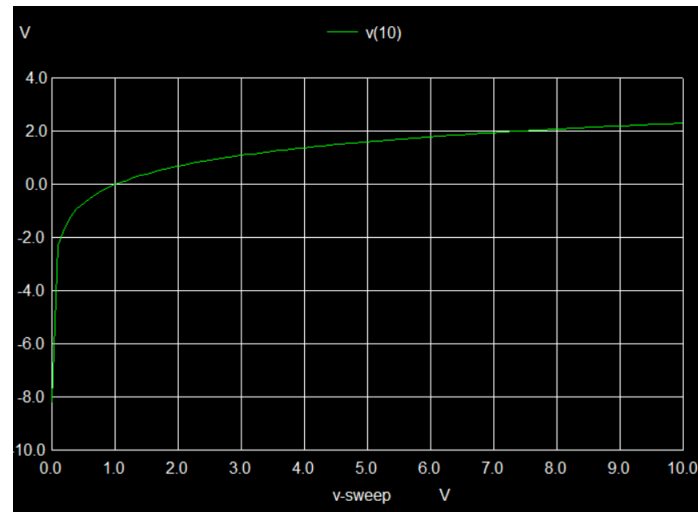


Figure 2:  $V_{out}$  vs  $V_{in}$  (ideal)

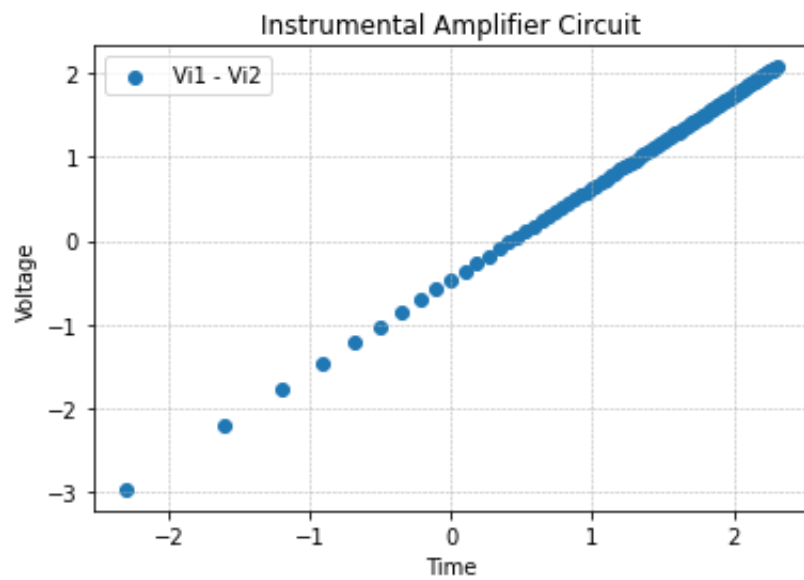


Figure 3:  $V_{out}$  vs  $\ln(V_{in})$  initially

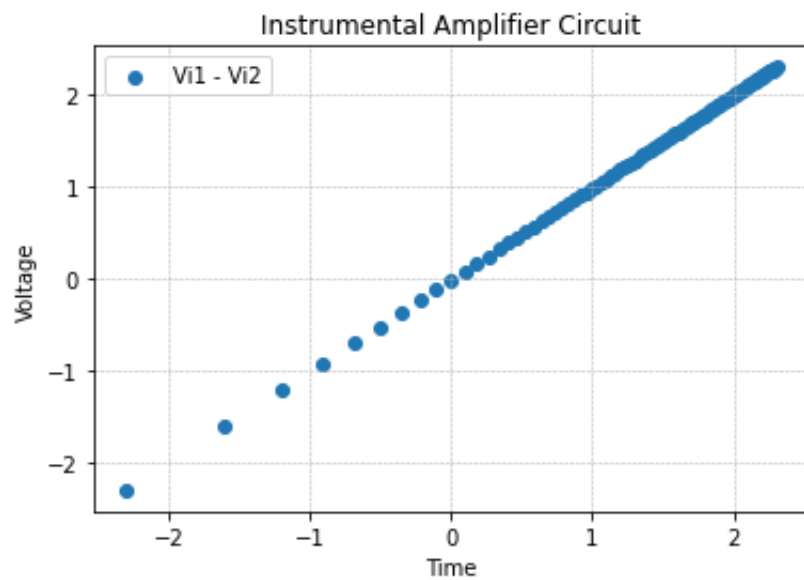


Figure 4:  $V_{out}$  vs  $\ln(V_{in})$  after refining (ideal)

## 4 Experimental results

Our value of  $V_{offset}$ , which came from the experimental IV data is -0.23V. But to make the  $V_{out}$  vs  $\ln(V_{in})$  graph to pass through (0,0), we have to make the  $V_{offset} = -0.219V$ .

To make the slope of this graph as 1, we had to change the value of  $R_2$  from  $1k\Omega$  (came by experimental analysis), to  $1.1k\Omega$ .

So, because of changing  $V_{offset}$  from -0.23V to -0.219V,  $a_2$  value changes from -0.46 to -0.438.

Due to changing of  $R_2$  from 1k to 1.1k,  $a_1$  value changes from -0.04862 to -0.05344.

## 5 Experiment completion status

All the parts of this experiment are completed successfully.